

Introduction to Electrical and Electronic Circuits

LAB. 6

Transmission line

Problems:

1. When a circuit has to be regarded as a circuit with distributed parameters i.e. as a transmission line?
2. When the transmission line is called:
 - a lossless line
 - a distortionless line(Explain the differences between voltage and current waveforms in these lines)
3. How can:
 - characteristic impedance Z
 - propagation velocity v
 - attenuation constantbe experimentally measured?
4. When the line is matched at the input and at the output?
5. Assume a lossless transmission line as shown in fig. 1. Draw $u(t,0)$, $i(t,0)$, $u(t,l/2)$, $i(t,l/2)$, $u(t,l)$, $i(t,l)$, $u(t_0/2, x)$, $i(t_0/2, x)$, $u(3t_0/2, x)$, $i(3t_0/2, x)$, $u(5t_0/2, x)$, $i(5t_0/2, x)$ where $t_0=1/v$ for every combination of the generator waveform $e(t)$, generator impedance Z_1 and load impedance Z_2 from the following:
 - $e(t)$
 1. constant source E switched on at $t=0$; $e(t)=E1(t)$
 2. a rectangular pulse of width $t_0/4$, $t_0/2$, t_0 , $3t_0/2$, $2t_0$
 3. a symmetrical triangle of width $t_0/4$, $t_0/2$, t_0 , $3t_0/2$, $2t_0$
 - $Z_1=0$; $Z/5$; Z ; $4Z$
 - $Z_2=0$ (short circuit); $Z/5$; Z (load match); $4Z$; open circuit; a capacitor C ; an inductor L ; a serial/parallel connection of a capacitor/inductor and a resistor $R=Z$.
 -

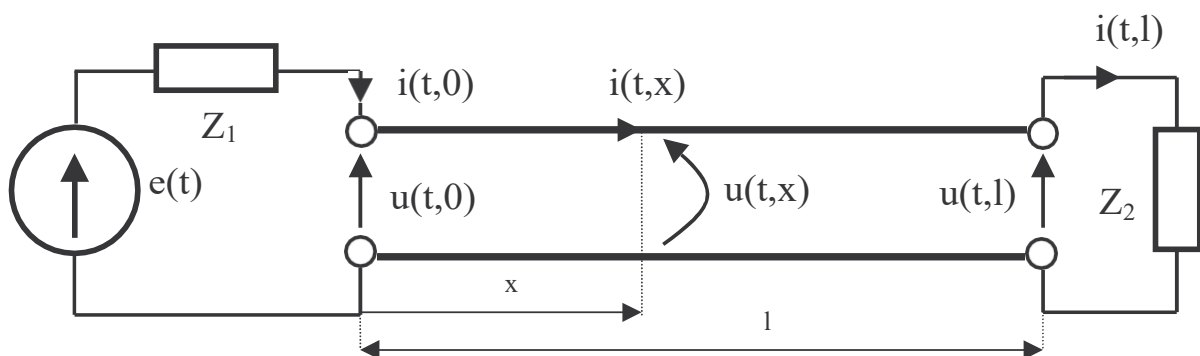


Fig. 1

Programme

Set the generator frequency $f_{\text{gen}}=1$ MHz. Make sure the pulses are symmetrical i.e. a duty factor is 1/2. Assemble a circuit shown in fig. 2. The set of plugs enables you to load the line with a number of different loads and to have a set of different input impedance values.

Generators used in this lab have an internal impedance $Z_{\text{gen}}=50\Omega$. To increase the input impedance over 50Ω you have to add some serial impedance Z_a . To decrease the input impedance below 50Ω you have to add some parallel impedance Z_b . A plug denoted with a single Ω figure may be used for Z_1 and Z_a while the only plug denoted with two Ω figures ($0/50\Omega$) is to be used for both Z_a and Z_b ($0/50\Omega$ meaning $Z_a=0\Omega$ and $Z_b=50\Omega$).

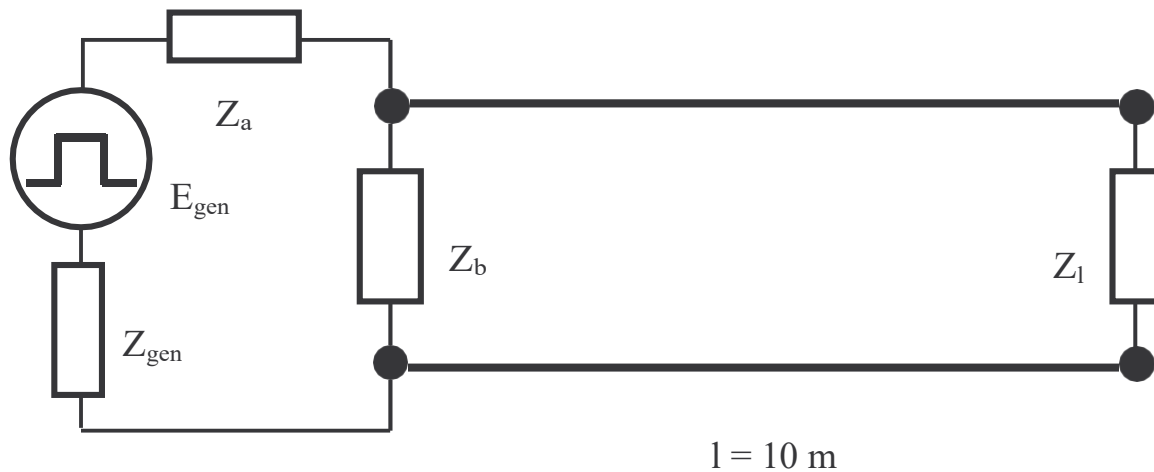


Fig. 2

1. Taking into account that line length $l=10$ m measure Z and v .
2. Observe voltages at line input and output for the following input and load impedances:
 - a). $Z_a=25\Omega$, $Z_l=\infty$ (line open)
 - b). $Z_a=25\Omega$, $Z_l=250\Omega$
 - c). $Z_a=25\Omega$, $Z_l=0$ (short circuit at the output)
 - d). $Z_a=25\Omega$, $Z_l = 1/SC$ (line loaded with a capacitor $C = 1.5$ nF)
 - e). $Z_a=0$, $Z_b=50\Omega$, $Z_l=\infty$ (line open)
 - f). $Z_a=0$, $Z_b=50\Omega$, $Z_l=0$ (short circuit at the output)
 - g). $Z_a=0$, $Z_b=50\Omega$, $Z_l=75\Omega$
 - h). $Z_a=250\Omega$, $Z_l=\infty$ (line open)
 - i). $Z_a=250\Omega$, $Z_l=0$ (short circuit at the output)
 - j). $Z_a=250\Omega$, $Z_l=75\Omega$
3. Check influence of oscilloscope cables and non-ideal pulse on observed waveforms.
4. Set $Z_a=0$, $Z_b=50\Omega$, $Z_l=\infty$ (line open) and f_{gen} so that pulse period equals $4l/v$ (or equivalently pulse width equal $2l/v$). Observe input and output voltages. (Set the trigger mode of the oscilloscope to the channel 2).

Report

1. Calculate v . Based on this estimate line primary parameters L and C (assume lossless line).
2. Draw observed waveforms (see items 2 and 4 in the "Programme" section) and compare them with theoretical calculations (also included and considered in the report).
3. Comment on item 3 in the "Programme" section.
4. Explain the waveforms observed at item 4.