

Theory of Logic Circuits					
Academic year	Term	Makrokierunek	Exercise Supervisor	Group	Section
2018/2019	Thursday 15:15-16:45		Exercise Supervisor	KP	1,2

Report from exercise number 1

Exercise performed on: 2019-03-21

Subject of the exercise:

Combinational switching circuits

Section consists of:

Mikołaj Dobosz group 1
Wojciech Bieniek group 2

Task 1


Design a switching circuit from given function $Z = \Sigma(0, 2, 4, 5, 6, 7, 8, 10, 15)_{x_3x_2x_1x_0}$.

$x_3x_2 \backslash x_1x_0$	00	01	11	10
00	1			1
01	1	1	1	1
11			1	
10	1			1

$$Z = \bar{x}_0\bar{x}_2 + \bar{x}_3x_2 + x_2x_1x_0$$

$$Z = \overline{\overline{\bar{x}_0\bar{x}_2 + \bar{x}_3x_2 + x_2x_1x_0}}$$

$$Z = \overline{\overline{\bar{x}_0\bar{x}_2} * \overline{\bar{x}_3x_2} * \overline{x_2x_1x_0}}$$

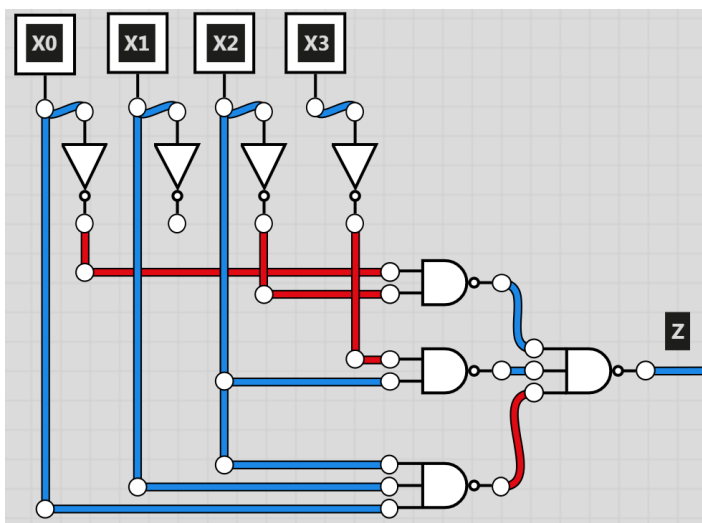

Task 2

Design a translator from the Gray code into the binary code.

Gray			Binary		
X ₂	X ₁	X ₀	Z ₂	Z ₁	Z ₀
0	0	0	0	0	0
0	0	1	0	0	1
0	1	1	0	1	0
0	1	0	0	1	1
1	1	0	1	0	0
1	1	1	1	0	1
1	0	1	1	1	0
1	0	0	1	1	1

x ₂ x ₁ \ x ₀	0	1
00	0	0
01	0	0
11	1	1
10	1	1

x ₂ x ₁ \ x ₀	0	1
00	0	0
01	1	1
11	0	0
10	1	1

x ₂ x ₁ \ x ₀	0	1
00	0	1
01	1	0
11	0	1
10	1	0

$$Z_0 = X_0 \bar{X}_2 \bar{X}_1 + \bar{X}_0 \bar{X}_2 X_1 + X_0 X_1 X_2 + \bar{X}_0 X_2 X_1$$

$$Z_0 = X_0 \oplus (X_1 \oplus X_2)$$

$$Z_0 = \overline{\overline{X_0 \bar{X}_1 \bar{X}_2} * \overline{\bar{X}_0 X_1 \bar{X}_2} * \overline{X_0 X_1 X_2} * \overline{\bar{X}_0 \bar{X}_1 X_2}}$$

$$Z_1 = \bar{X}_2 X_1 + X_2 \bar{X}_1$$

$$Z_1 = X_1 \oplus X_2$$

$$Z_1 = \overline{\overline{X_1 \bar{X}_2} * \overline{\bar{X}_1 X_2}}$$

$$Z_2 = X_2$$

