

Theory of Logic Circuits					
Academic year	Term		Exercise Supervisor	Deans group	Section
2018/2019	Tuesday	Makrokierunek	Krzysztof Paszek	1,2	1
	15:00 – 17:45				

Report from exercise number 3

Exercise performed on: 2019-03-06

Subject of the exercise:

Bistable devices


Section consists of:

Wojciech Bieniek, gr. 2

Mikołaj Dobosz, gr. 1

 Task 1

Design and implement with NAND gates sr basic latch with dominant setting input. Draw timing diagrams (taken from the built circuit) illustrating the behaviour of the device.



Our method:

To start building the gate, we wrote two Karnaugh Maps $q/s/r$ for Q and $q/s/r$ for $\sim Q$, based on excitation table for SR with S dominance (included in point 1.2 of introductory pdf).

q \ sr	00	01	11	10
00	1	1	1	0
01	0	1	1	0

$$\bar{Q} = r + \bar{q}\bar{s} \quad \sim Q$$

q \ sr	00	01	11	10
00	0	0	1	1
01	1	0	1	1


$$Q = q\bar{r} + s \quad Q$$

Next, we had to modify our results to fit it to the lab's equipment. Using double negation and logical transformations, we can compose Q and $\sim Q$ of NAND gates.


$$\bar{Q} = \overline{\overline{\overline{r}\overline{q}\overline{s}}}$$

$$Q = \overline{\overline{\overline{q}\overline{r}\overline{s}}}$$

 With those we proceeded to building the circuit.



 When testing the circuit, this is the timing diagram we've observed:




In state 6 we can see, that while there is no signal on either s or r , the output remains set. What was unexpected though, is the fact that not only was Q set, but so was $\sim Q$. This is natural behaviour for NAND gates, which are both provided with '0' on input, but an undefined state for SR latch.

Task 3


Use only asynchronous inputs of the synchronous D flip-flop to determine their active value and which of them is dominant. Draw timing diagrams used to resolve the problem.

Our method:

 We've used the JK gate available in the lab, with J , K , $\sim S$ and $\sim R$ inputs. Leaving J and K floating, we plugged $\sim S$ and $\sim R$ to respective buttons' negated output.



 When testing different input combinations, this is the timing diagram we saw:




Here, we can notice the reaction opposite to the SR gate from the first task. When both inputs are absent, the **Q**, as well as **~Q** are '0'. This means that JK's asynchronous inputs are reset-dominant.

Task 5

Recognise the triggering way of the synchronous D flip-flops (gated latch, master slave with or without 1s and 0s catching, or positive or negative edge-triggered). Draw timing diagrams used to resolve the problem.

Our method:

 While inspecting the D gate, we run the same input combination as in previous tasks on it, in order to determine the triggering way. This is what we observed:



From this diagram, we can evaluate that **D gate is triggered by the CLK's rising edge**. On such occurrence, it reads the state of **D** input and rewrites it to **Q**, until next **CLK**'s rising edge.

