

Theory of Logic Circuits						
Academic year	Term	Makrokierunek	Exercise Supervisor	Group	Section	
2018/2019	Thursday		Exercise Supervisor	KP	3	1
	15:15-16:45					

Report from exercise number 4

Exercise performed on: 2019-04-25


Subject of the exercise:
Asynchronous sequential logic circuits

Section consists of:

Mikołaj Dobosz
Wojciech Bieniek

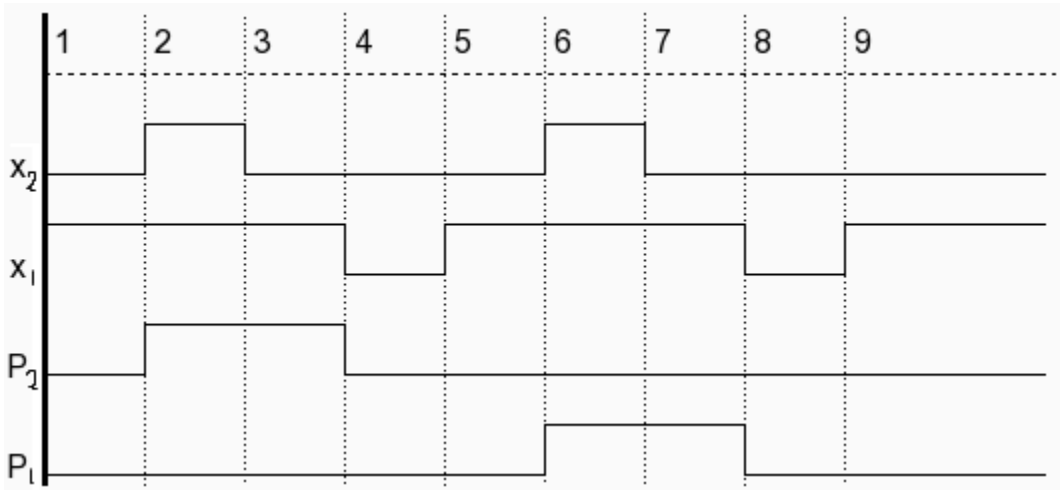Task 1

Implement with chosen by the supervisor elements (with or without sr latches), a circuit controlling the switching of two pumps. The pumps P1 and P2 (see fig.1) should be switched on alternately (only one pump can work at a time) when water exceeds the level of the sensor x2 (i.e. when x2 = 1). Working pump should be switched off when the water level is below the sensor x1 (i.e. when x1 = 0). Assume that water level grows when pumps are off, and that it decreases when any pump is working.



x1x2	00	01	11	10	P1P2
0			1	0	00
1			1	2	01
2	3			2	01
3	3			4	00
4			5	4	00
5			5	6	10
6				6	10
7	7			0	00

q1q2 \ x1x2	00	01	11	10	P1P2
00	7		1	0	00
01	3		1	2	01
11	3		5	4	00
10	7		5	6	10

q1q2\x1x2	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	1	1	1	1
10	0	1	1	1

Q1

q1q2\x1x2	00	01	11	10
00	0	1	0	0
01	1	1	1	1
11	1	0	0	1
10	0	0	0	0

Q2

$$Q_1 = Q_2 \bar{x}_1 + Q_1 Q_2 + x_1 Q_1$$

$$\bar{S}_1 = \bar{Q}_2 \bar{x}_1$$

$$\bar{R}_1 = \bar{Q}_2 \bar{x}_1$$

$$Q_2 = Q_2 \bar{x}_2 + x_2 \bar{Q}_1 + Q_1 Q_2 = \bar{Q}_2 \bar{x}_2 * x_2 \bar{Q}_1 * Q_1 Q_2$$

$$\bar{S}_2 = \bar{Q}_1 x_2$$

$$\bar{R}_2 = \bar{Q}_1 x_2$$

Q1\Q2	0	1
0	0	0
1	1	0


P1

Q1\Q2	0	1
0	0	1
1	0	0

P2

$$P1 = Q1 \bar{Q}_2 = \bar{Q}_1 + Q_2$$

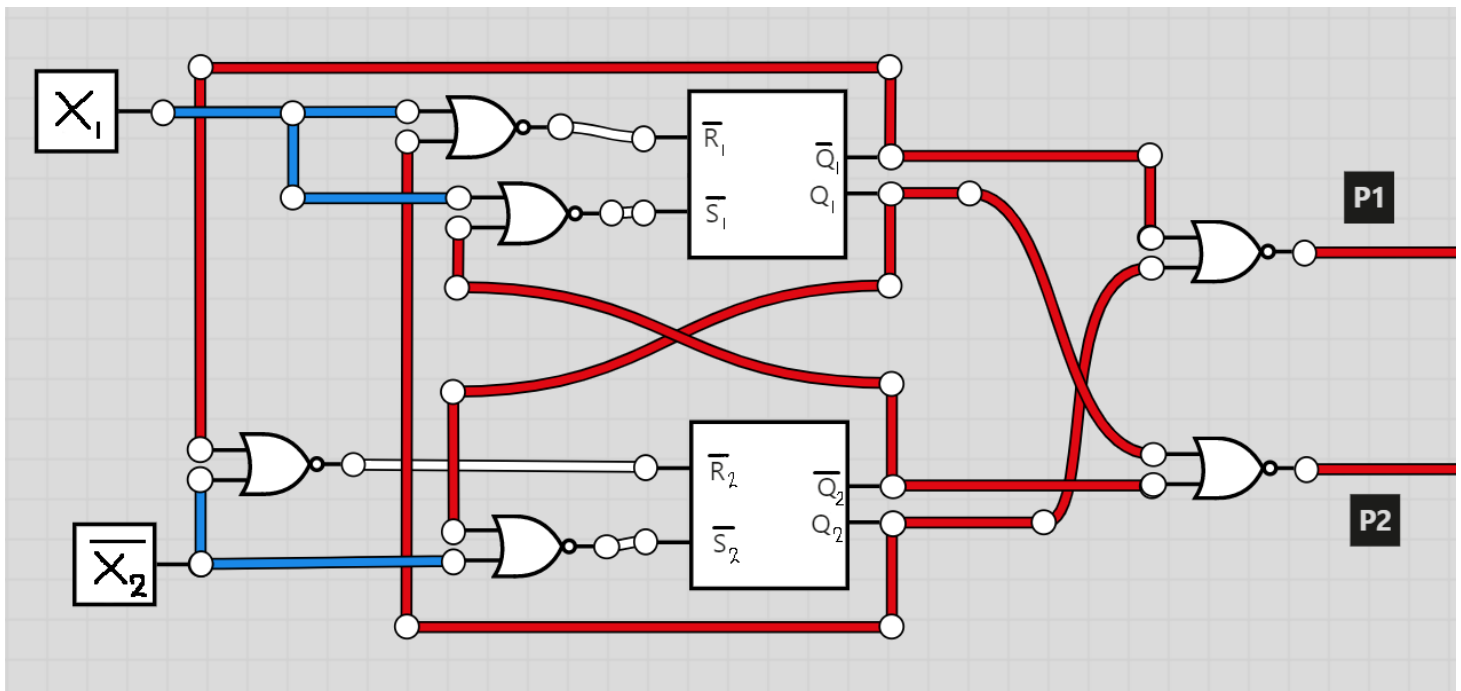
$$P2 = \bar{Q}_1 Q_2 = \bar{Q}_1 + \bar{Q}_2$$



Sorry about those upside-down flip-flops!

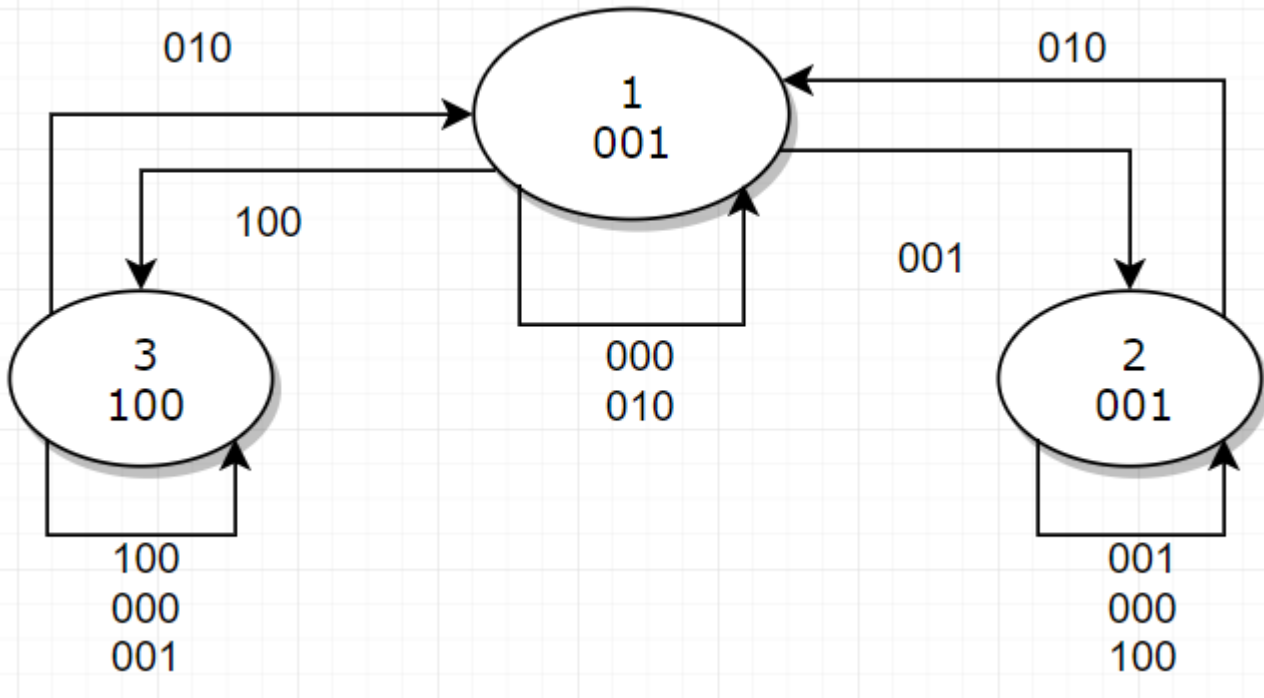Task 2

Implement with chosen by the supervisor elements (with or without sr latches), a circuit controlling the operation of the inertial two-directional engine (fig 2). The engine can start to rotate only if it is stopped (RIGHT = 0, LEFT = 0, STOP = 1). The engine should start to rotate in right direction (RIGHT = 1) when button R is pressed for a short moment and it should keep rotating until button S is pressed. Pressing the R or L button when engine rotates right should be ignored. The engine should start to rotate in left direction (LEFT = 1) when button L is pressed for a short moment and it should keep rotating until button S is pressed. Pressing the L or R button when engine rotates left should be ignored. Similarly pressing S button when engine is stopped should not change its state. Pressing it when engine rotates in any direction should stop it by assigning outputs: RIGHT = 0, LEFT = 0, STOP = 1. Since all input buttons are monostable radio ones, it is assumed that only one of buttons S, L, R can be equal to one at a time.



xr xs xl	00	01	11	10
000	0	0	1	
001	0	1	1	
011				
010	0	0	0	
110				
111				
101				
100	0	0	1	

Q1

xr xs xl	00	01	11	10
000	0	1	1	
001	0	1	1	
011				
010	1	1	1	
110				
111				
101				
100	0	0	1	

Q2

$$\overline{s_1} = \overline{Q_2 x_L}$$

$$\overline{r_1} = \overline{x_S}$$

$$\overline{s_2} = \overline{x_S}$$

$$\overline{r_2} = \overline{Q_1 x_R}$$

Q1\Q2	0	1
0	1	0
1		0

Y_R

Q1\Q2	0	1
0	0	1
1		0

Y_S

Q1\Q2	0	1
0	0	0
1		1

Y_L

$$Y_R = \overline{Q_2}$$

$$Y_S = \overline{Q_1}Q_2 = \overline{Q_1 + \overline{Q_2}}$$

$$Y_L = Q_1$$

